

Technician Licensing Class

Go Picture
Presented by
These!



TECHNICIAN CLASS GENERAL CLASS EXTRA CLASS

TECHNICIAN CLASS

FCC Element 2 Amateur Radio License Preparation



Contains the complete 394-question FCC Element 2 question pool effective July 1, 2010 to June 30, 2014
by GORDON WEST, W8AQA



- Fully-illustrated Text: Aids Learning
- Questions Reorganized for Logical Easy Learning
- Highlighted Key Words in Answer Explanations
- Easy Educational Explanations: Teach You Ham Radio
- Over 125 Addresses of Helpful Educational Websites
- Frequency Chart Showing Privileges
- Chapter on Learning Morse Code
- List of VEC Examiners

Includes BONUS COUPONS!
FREE Q MAGAZINE TRIAL SUBSCRIPTION
FREE BOOK WITH ARL MEMBERSHIP
DISCOUNT ON YOUR FIRST RADIO!



Amateur Radio Technician Class Element 2 Course Presentation

➤ **ELEMENT 2 SUB-ELEMENTS** (Groupings)

- **About Ham Radio**
- **Call Signs**
- **Control**
- **Mind the Rules**
- **Tech Frequencies**
- **Your First Radio**
- **Going On The Air!**
- **Repeaters**
- **Emergency!**
- **Weak Signal Propagation**

Amateur Radio Technician Class Element 2 Course Presentation








➤ **ELEMENT 2 SUB-ELEMENTS** (Groupings)

- **Talk to Outer Space!**
- **Your Computer Goes Ham Digital!**
- **Multi-Mode Radio Excitement**
- **Run Some Interference Protection**
- **Electrons - Go With the Flow!**
- **It's the Law, per Mr. Ohm!**
- **Go Picture These!**
 - **Antennas**
 - **Feed Me with Some Good Coax!**
 - **Safety First!**

Go Picture These!

- T6C1 Schematic symbols is the name for standardized representations of components in an electrical wiring diagram.


Schematic Symbols

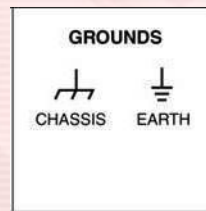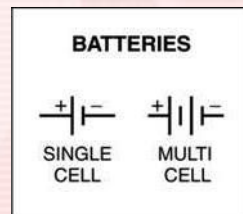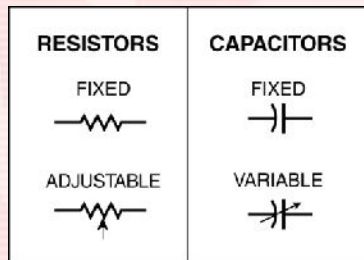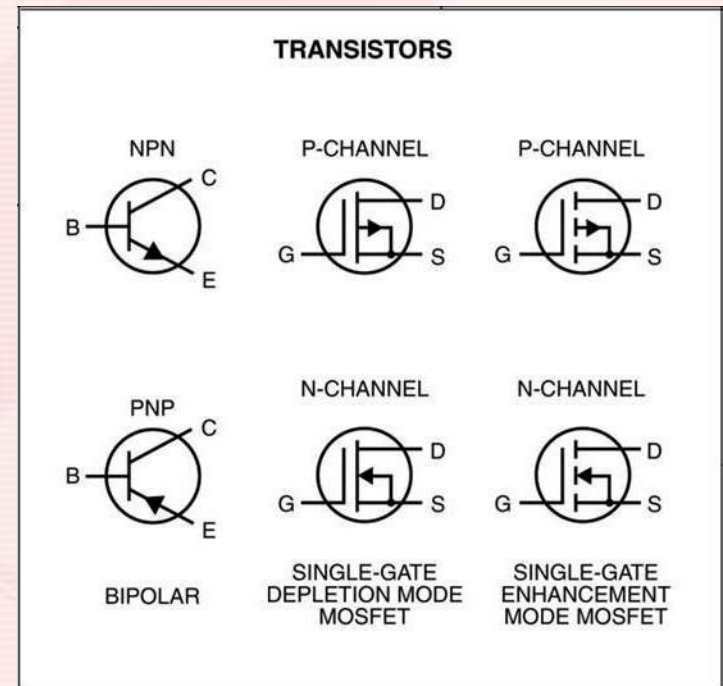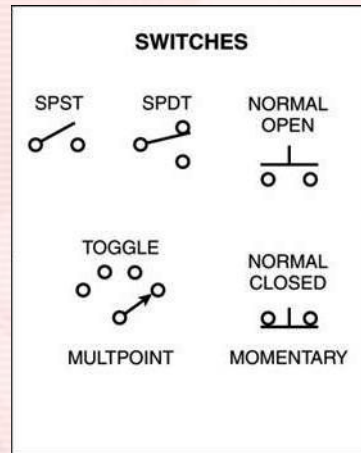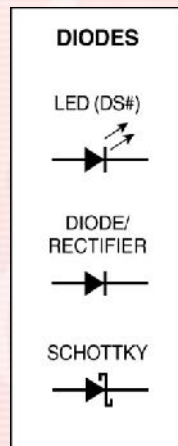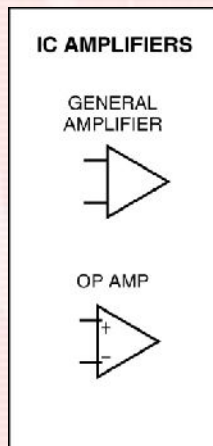

Go Picture These!

Schematic Symbols


LOGIC (U#)

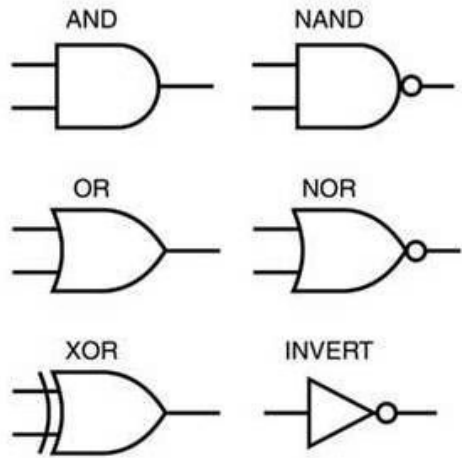


INDUCTORS



RELAYS

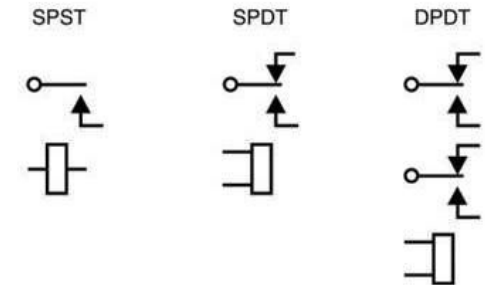


ANTENNA

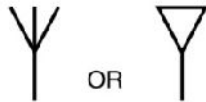

OR

SPEAKER CRYSTAL

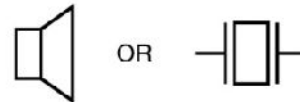


OR

- T6C12 The symbols on an electrical circuit schematic diagram represent electrical components.

Go Picture These!

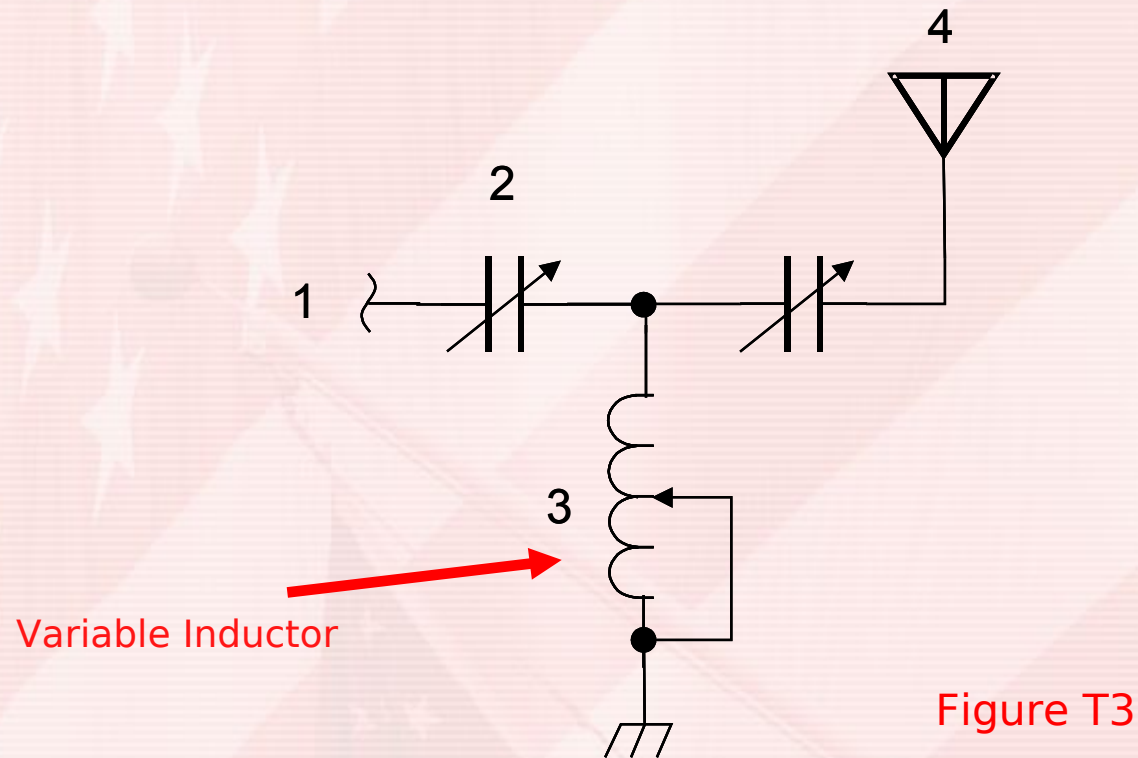- T6C10 Component 3 in figure T3 is a variable inductor.



Go Picture These!

- T6C11 Component 4 in figure T3 is an antenna.


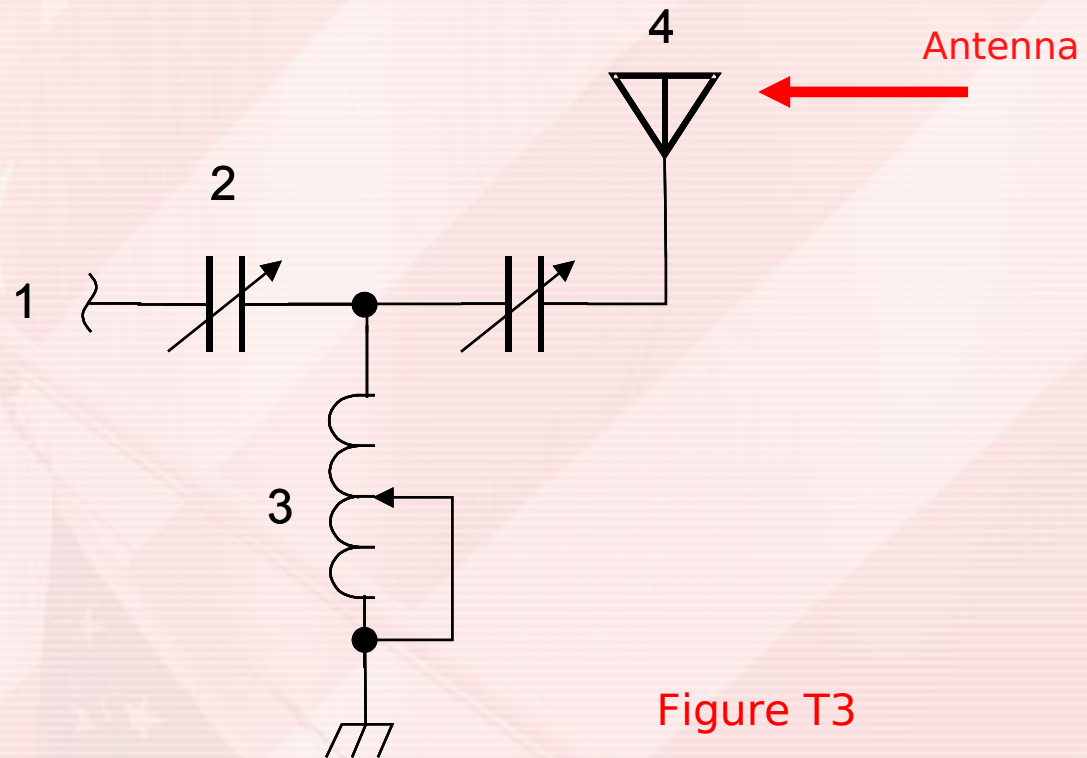


Figure T3


Go Picture These!

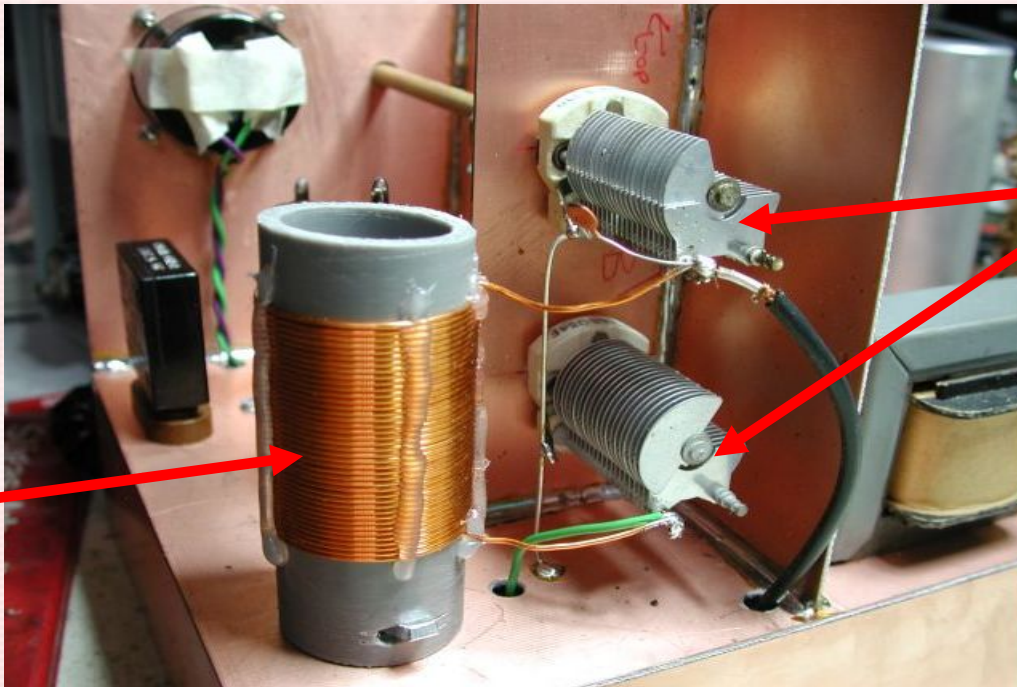- T6D8 A capacitor is used together with an inductor to make a tuned circuit.



Inductor

Capacitor
(variable)

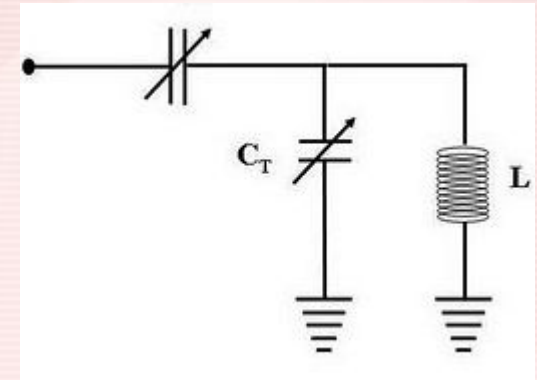

Tank Circuit Schematic

Tank Circuit or Tuned Circuit

Go Picture These!

T6C2 Component 1 in figure T1 is a resistor.

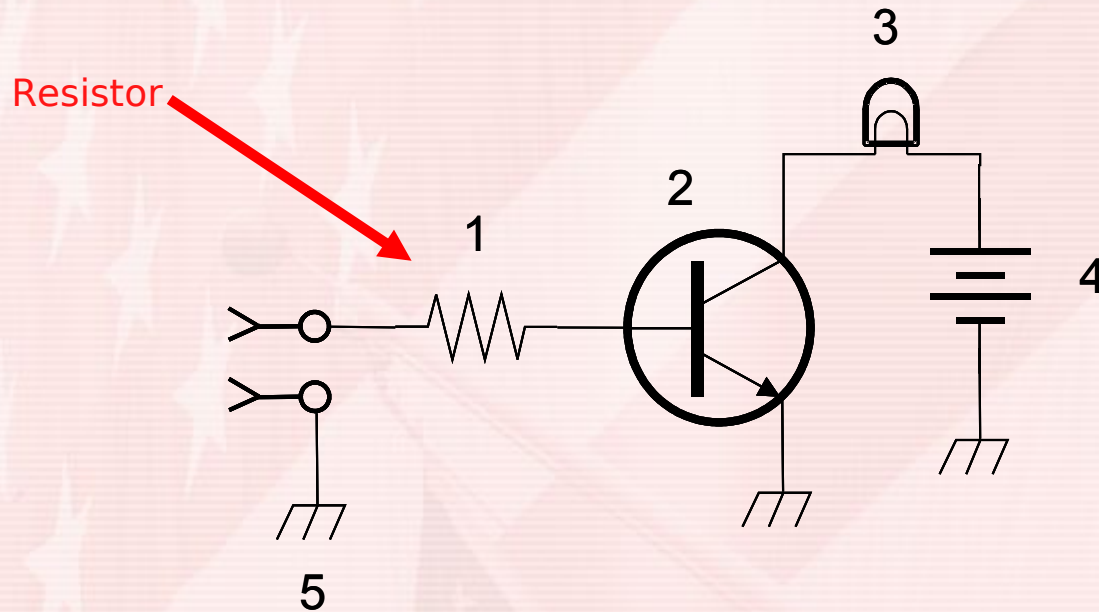


Figure T1

Go Picture These!

- T6C3 Component 2 in figure T1 is a transistor.


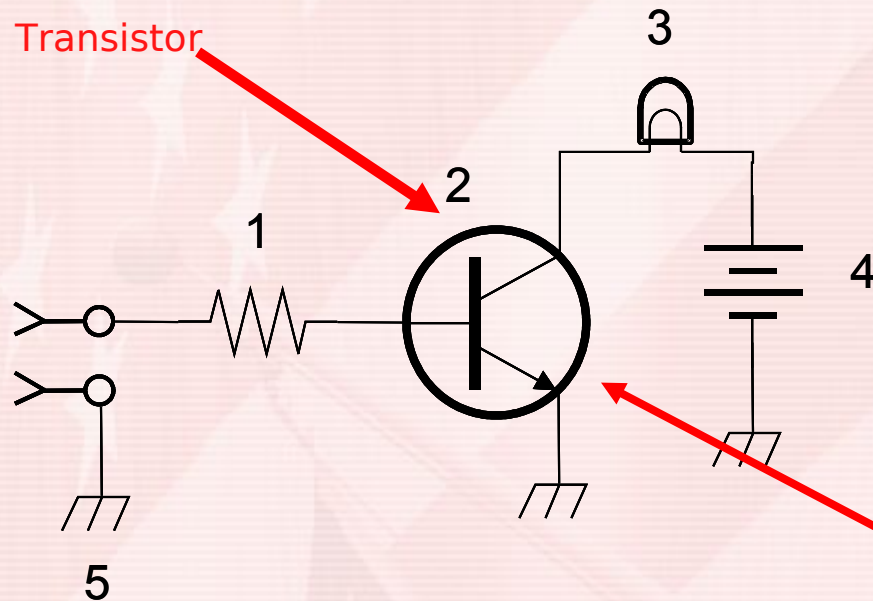


Figure T1

- T6D10 To control the flow of current is the function of component 2 in Figure T1.

Go Picture These!

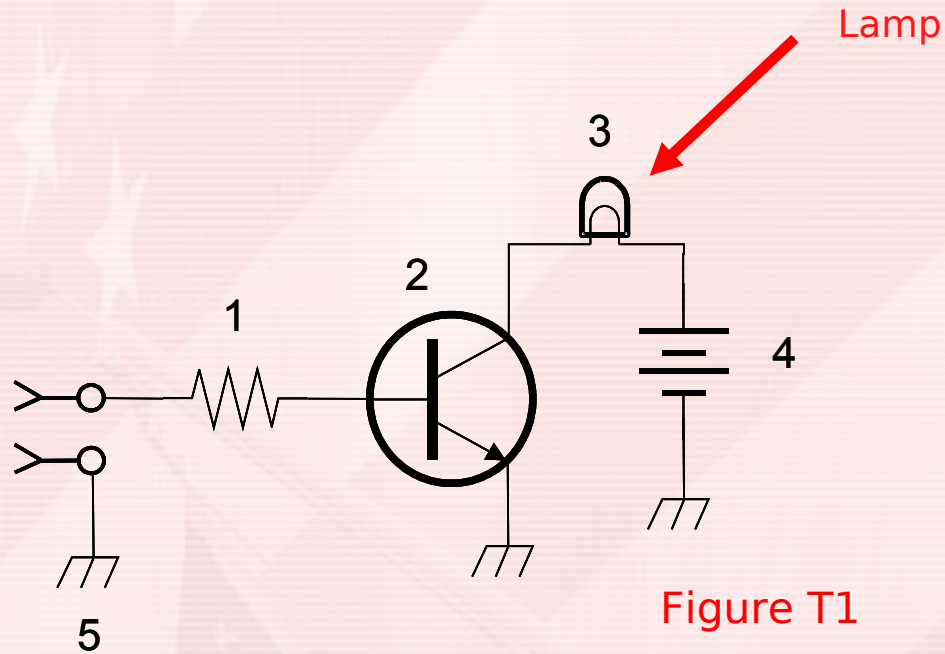- T6C4 Component 3 in figure T1 is a lamp.



Go Picture These!

- T6C5 Component 4 in figure T1 is a battery.

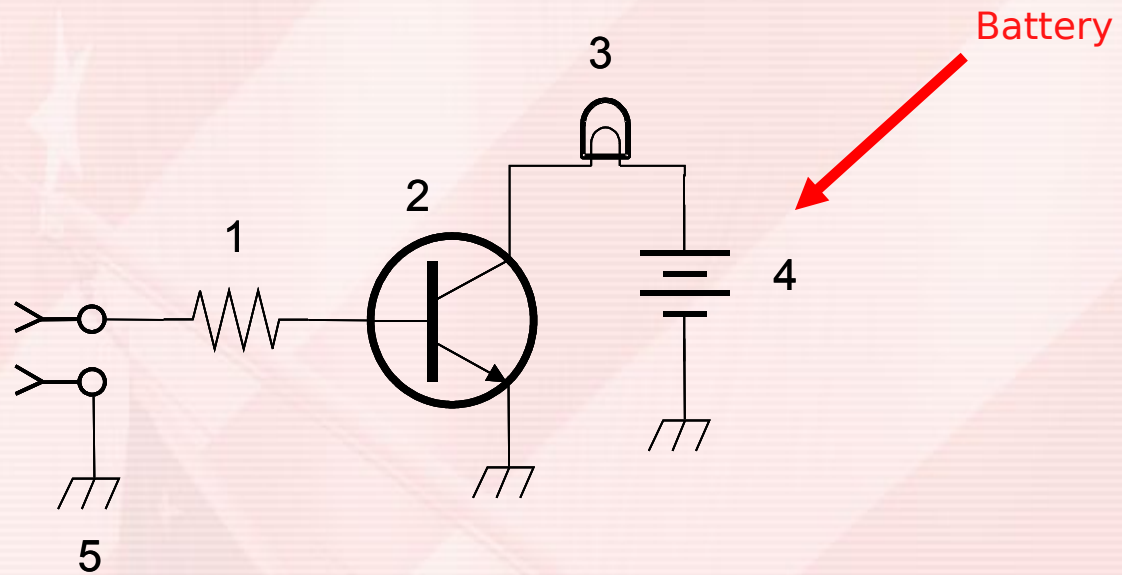


Figure T1

Go Picture These!

- T6D3 A single-pole single-throw switch is represented by item 3 in figure T2.


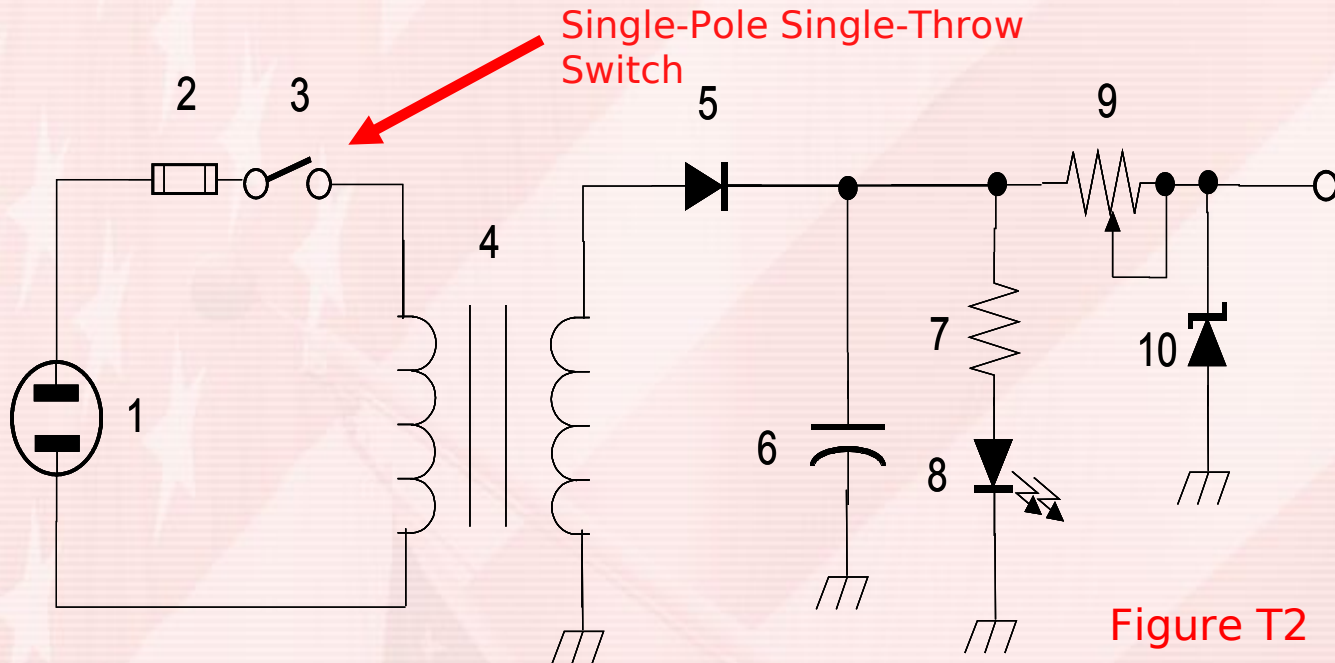


Figure T2

Go Picture These!

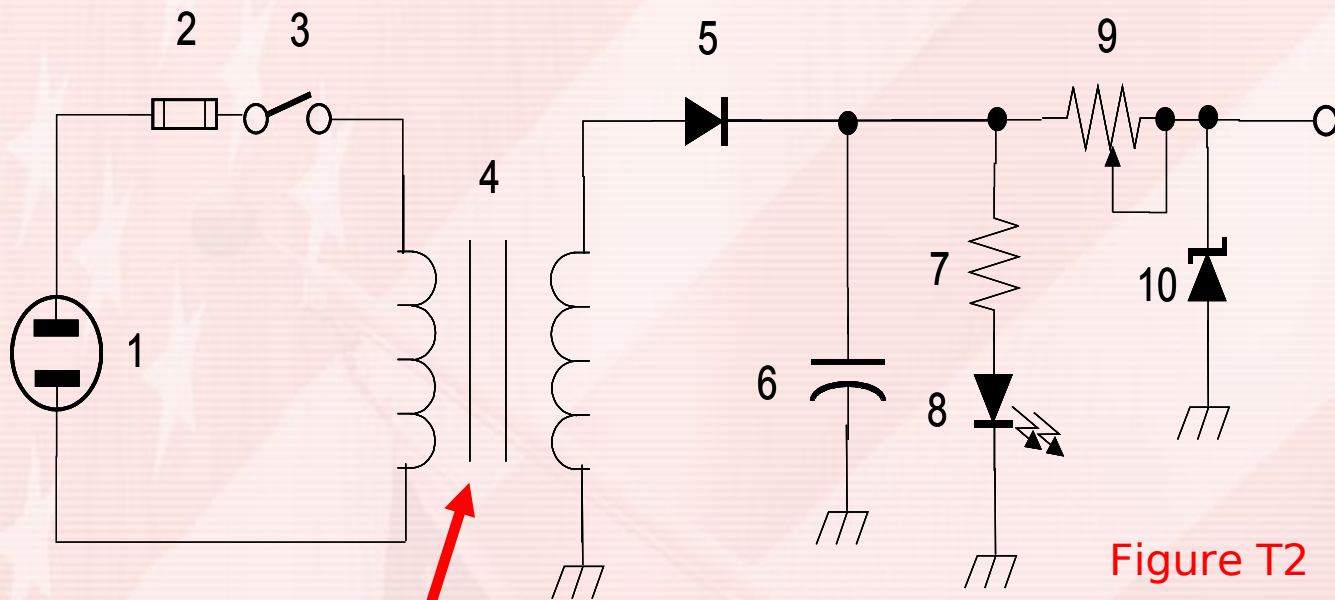- T6C9 Component 4 in figure T2 is a transformer.




Transformer

Figure T2

Go Picture These!

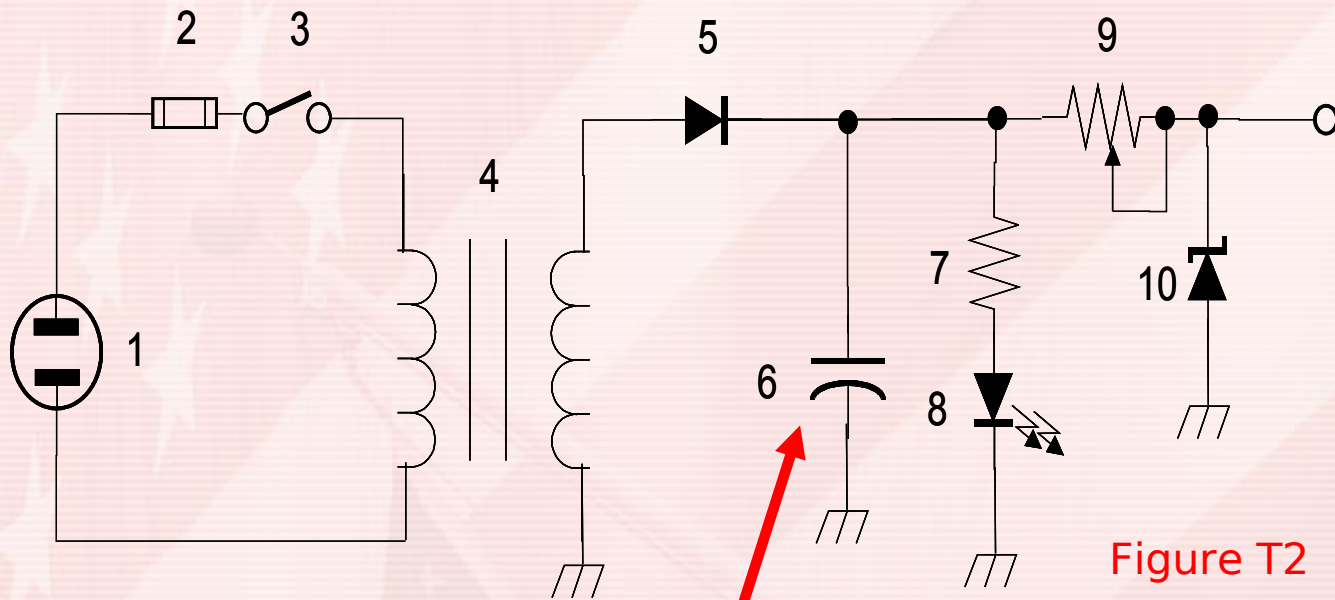- T6C6 Component 6 in figure T2 is a capacitor.



Capacitor

Figure T2

Go Picture These!

- T6C7 Component 8 in figure T2 is a light emitting diode.


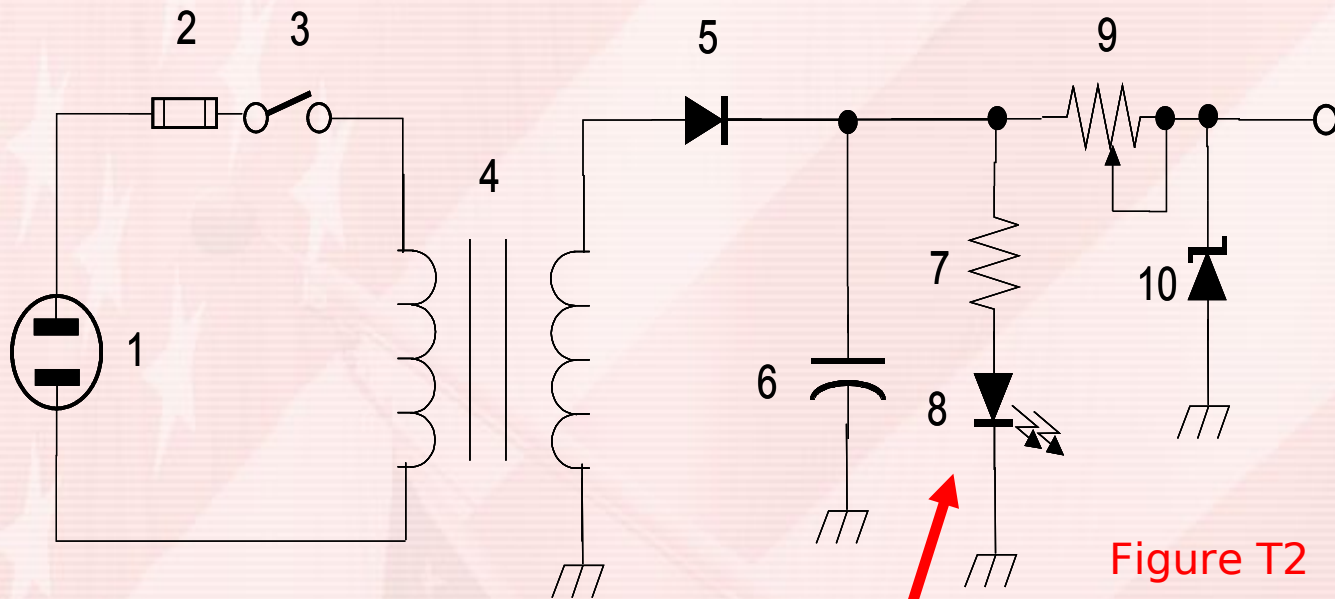


Figure T2

Light Emitting Diode

Go Picture These!

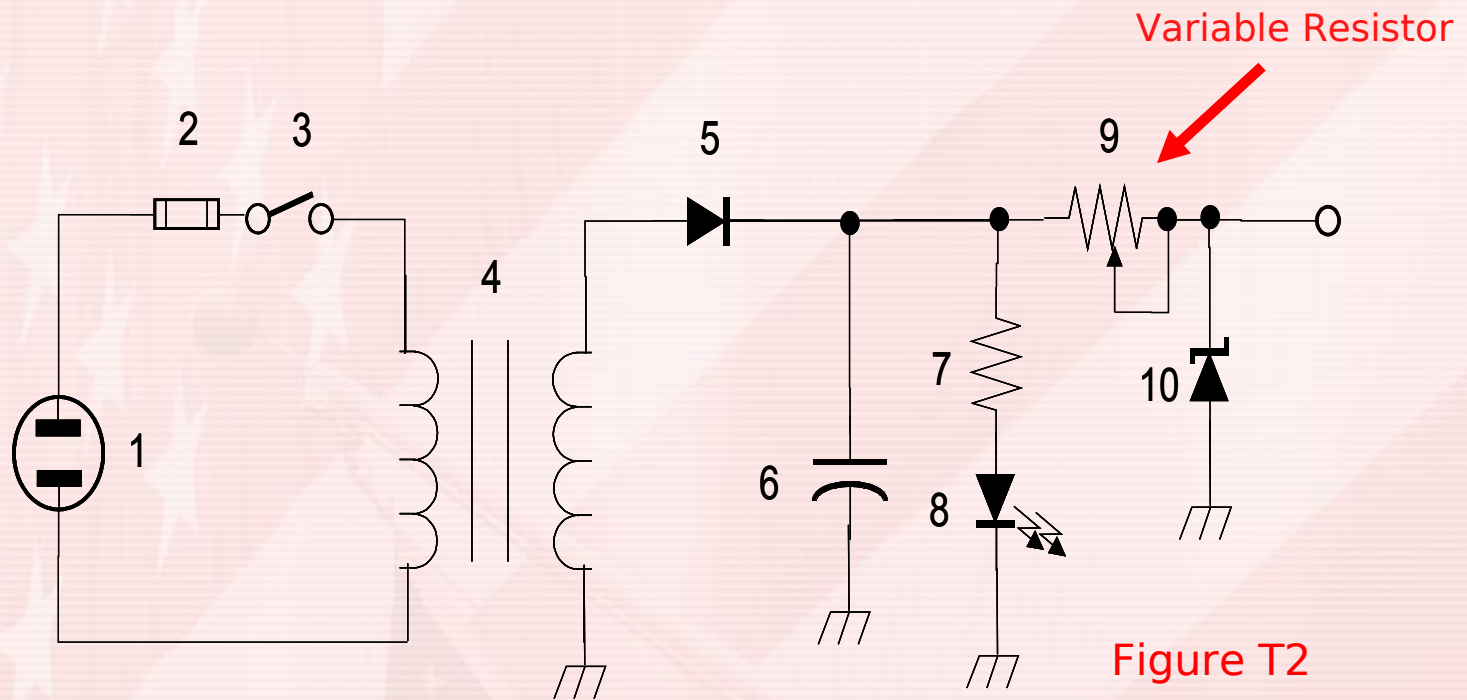- T6C8 Component 9 in figure T2 is a variable resistor.



Go Picture These!

- T6D4 A meter can be used to display signal strength on a numeric scale.



S-Meter



Icom 7600





Icom 7800


Go Picture These!

T6D2 A switch controlled by an electromagnet best describes a relay.

Relays

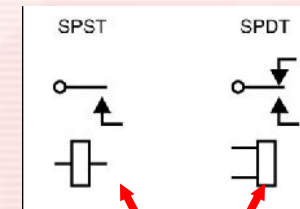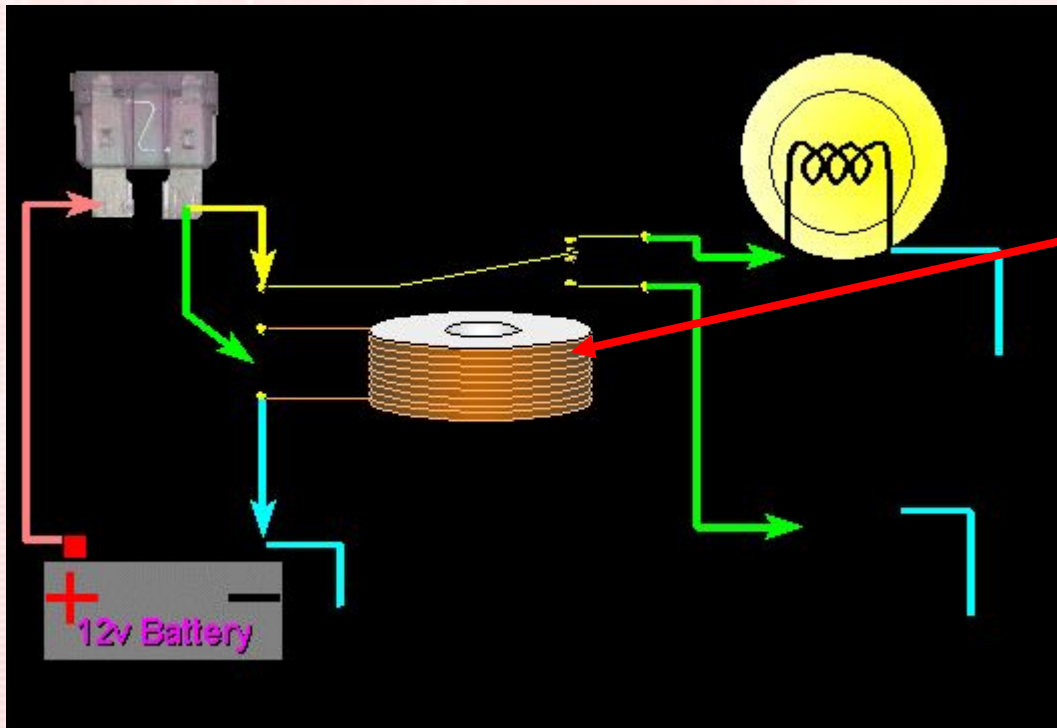

Electromagnet
S

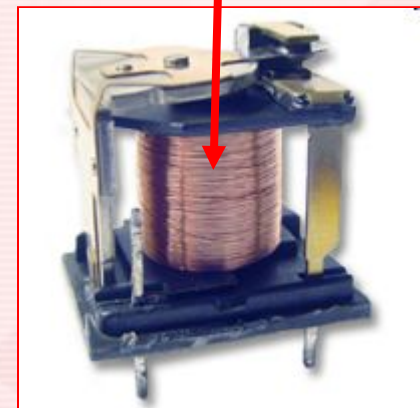

Go Picture These!

- T5B9 The approximate amount of change, measured in decibels (dB), of a power increase from 5 watts to 10 watts is 3dB.
 - 3 dB gain is a double of power

<u>dB</u>	<u>Power Change</u>
3 dB	2x Power
6 dB	4x change
9 dB	8x Power
10 dB	10x change
20 dB	100x Power
30 dB	1000x change
40 dB	10,000x Power change

Derivation:

If $\text{dB} = 10 \log_{10} \frac{P_1}{P_2}$

then what power ratio is 20 dB?

$$20 = 10 \log_{10} \frac{P_1}{P_2}$$

$$\frac{20}{10} = \log_{10} \frac{P_1}{P_2}$$

$$2 = \log_{10} \frac{P_1}{P_2}$$

Remember: logarithm of a number is the exponent to which the base must be raised to get the number.

$$\therefore 10^2 = \frac{P_1}{P_2}$$

$$100 = \frac{P_1}{P_2}$$

Or $P_1 = 100 P_2$

20 dB means P_1 is 100 times P_2

- T5B10 The approximate amount of change, measured in decibels (dB), of a power decrease from 12 watts to 3 watts is 6dB.
- T5B11 The approximate amount of change, measured in decibels (dB), of a power increase from 20 watts to 200 watts is 10 dB.

Go Picture These!

- T6D5 A regulator is a type of circuit that controls the amount of voltage from a power supply.




Voltage Regulators

- T6D6 A transformer is a component commonly used to change 120V AC house current to a lower AC voltage for other uses.



Voltage Transformer


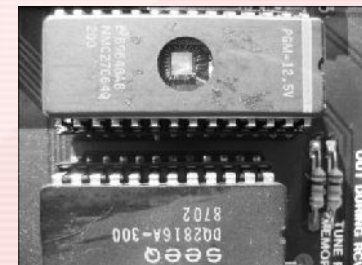
- T6D9 Integrated circuit is the name of a device that combines several semiconductors and other components into one package.




Large-scale integrated circuit chips .

Go Picture These!

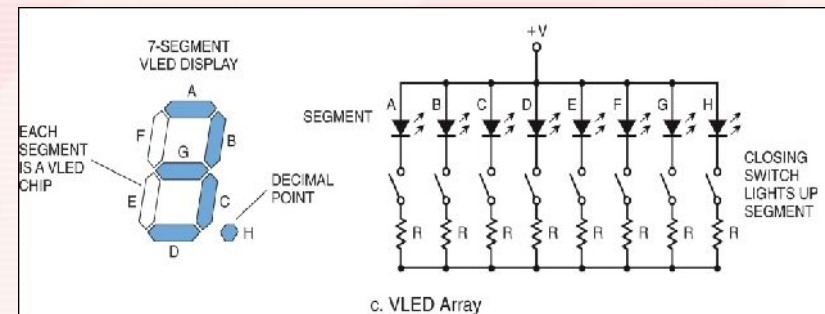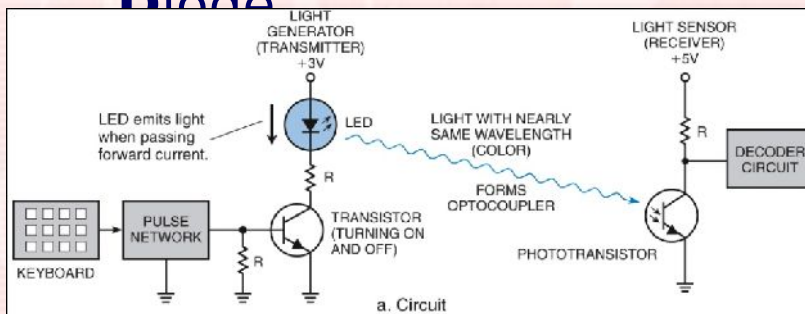- T6B7 The abbreviation "LED" stands for **L**ight **E**mitting **D**iode



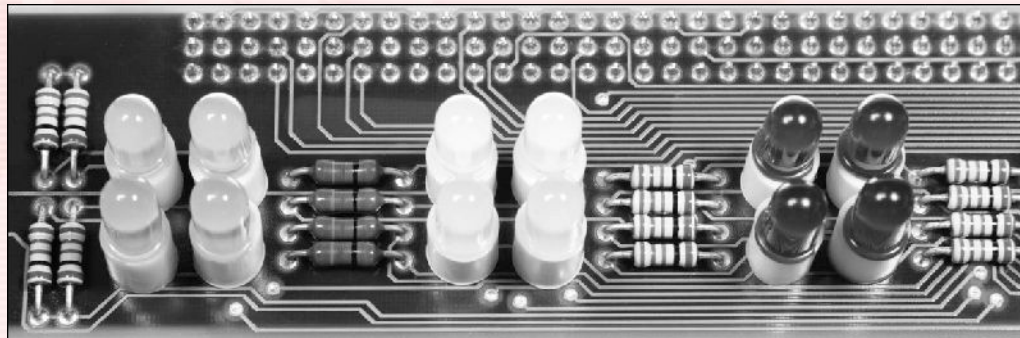- T6D7 An LED is commonly used as a visual indicator.



An array of LEDs and resistors mounted on a printed circuit board

Go Picture These!

- T5B2 1500 kHz is another way to specify a radio signal frequency of 1,500,000 hertz.
- T5B3 One thousand volts are equal to one kilovolt.
- T5B6 If an ammeter calibrated in amperes is used to measure a 3000-milliampere of current, the reading would it to be 3 amperes.

Scientific Notation			
Prefix Factor	Multiplication Factor	Prefix	Multiplication
tera	10^{12}	1,000,000,000,000	0.1
giga	10^9	1,000,000,000	0.01
mega	10^6	1,000,000	0.001
kilo	10^3	1,000	0.000001
hecto	10^2	100	0.00000001
deca	10^1	10	0.000000000001
unit	10^0	1	0.0000000000000001
			0.1
			0.01
			0.001
			0.000001
			0.00000001
			0.000000000001
			0.0000000000000001

Go Picture These!

<u>Metric</u> <u>English</u>	<u>Exponent</u>	
Tera	10^{12}	Trillion
Giga	10^9	Billion
Mega	10^6	Million
Kilo	10^3	Thousand
Centi	10^{-2}	Hundredth
Milli	10^{-3}	Thousandth
Micro	10^{-6}	Millionth
Nano	10^{-9}	Billionth
Pico	10^{-12}	Trillionth

- T5B5 0.5 watts is equivalent to 500 milliwatts.
- T5B1 1,500 milliamperes is 1.5 amperes.
- T5B8 One microfarads is equal to 1,000,000 picofarads.
- T5B4 One one-millionth of a volts is equal to one microvolt

Go Picture These!

- T7D8 Rosin-core solder is best for radio and electronic use.
- T7D9 A grainy or dull surface is the characteristic appearance of a "cold" solder joint.
- T7D7 Voltage and resistance are measurements commonly made using a multimeter.



Volt Ohm Meter VOM

<u>Parameter Instrument</u>	<u>Basic Unit</u>	<u>Measuring</u>
Voltage (E)	Volts	Voltmeter
Current (I)	Amperes	Ammeter
Resistance	Ohms 10^3	Ohmmeter
Power (P)	Watts	Wattmeter



Digital Volt Ohm Meter
Much more accurate

Go Picture These!

- T7D11 A precaution taken when measuring circuit resistance with an ohmmeter is to ensure that the circuit is not powered.
- T7D6 Attempting to measure voltage when using the resistance setting might damage a multimeter.
- T7D10 When an ohmmeter is connected across a circuit and initially indicates a low resistance and then shows increasing resistance with time, the circuit contains a large capacitor.

Learning how to use
a multimeter is an
essential skill in
testing and repairing
radio gear



Element 2 Technician Class Question Pool

Go Picture These!

Valid July 1, 2010

Through

June 30, 2014



T6C01

What is the name for standardized representations of components in an electrical wiring diagram?

- A. Electrical depictions
- B. Grey sketch
- C. Schematic symbols
- D. Component callouts

16C12 What do the symbols on an electrical circuit schematic diagram represent?

- A. Electrical components
- B. Logic states
- C. Digital codes
- D. Traffic nodes

T6C13 Which of the following is accurately represented in electrical circuit schematic diagrams?

- A.** Wire lengths
- B.** Physical appearance of components
- C.** The way components are interconnected
- D.** All of these choices

T6C10 What is component 3 in figure T3?

- A. Connector
- B. Meter
- C. Variable capacitor
- D. Variable inductor


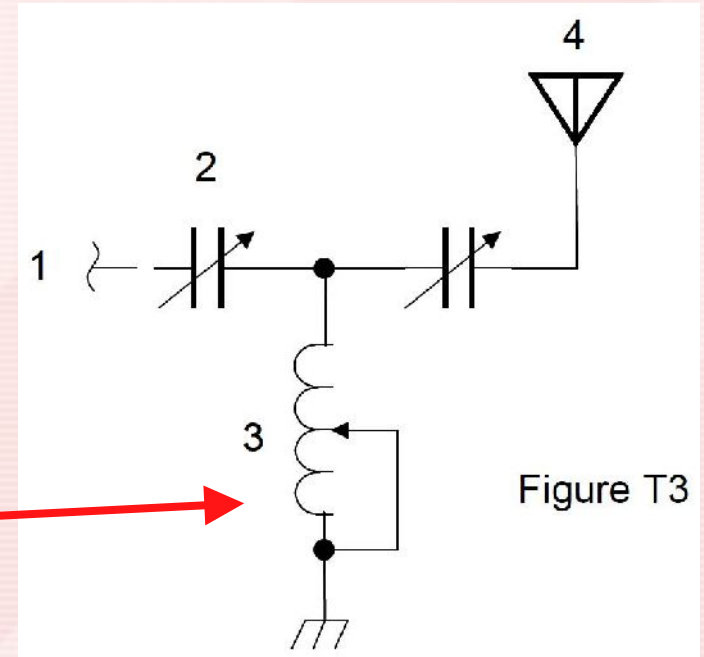


Figure T3

T6C11 What is component 4 in figure T3?

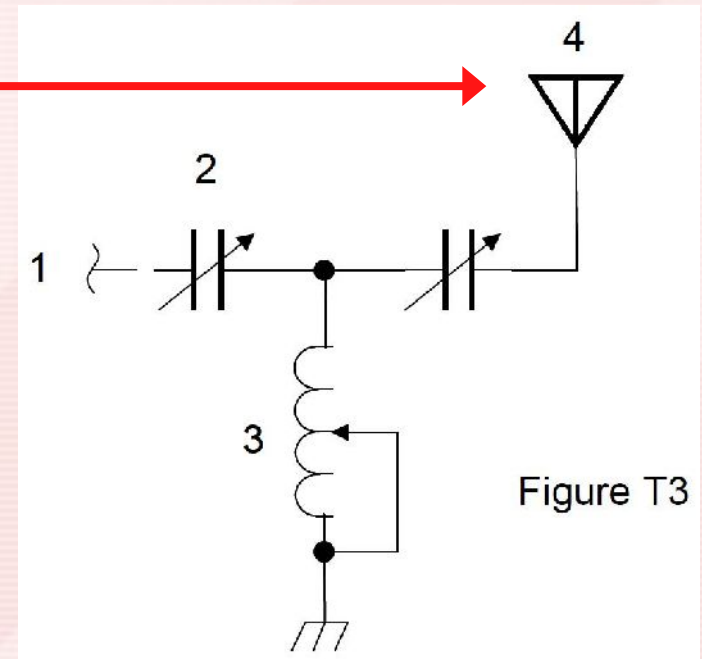- A. Antenna
- B. Transmitter
- C. Dummy load
- D. Ground




16D08 Which of the following is used together with an inductor to make a tuned circuit?

- A. Resistor
- B. Zener diode
- C. Potentiometer
- D. Capacitor


T6C02 What is component 1 in figure T1?

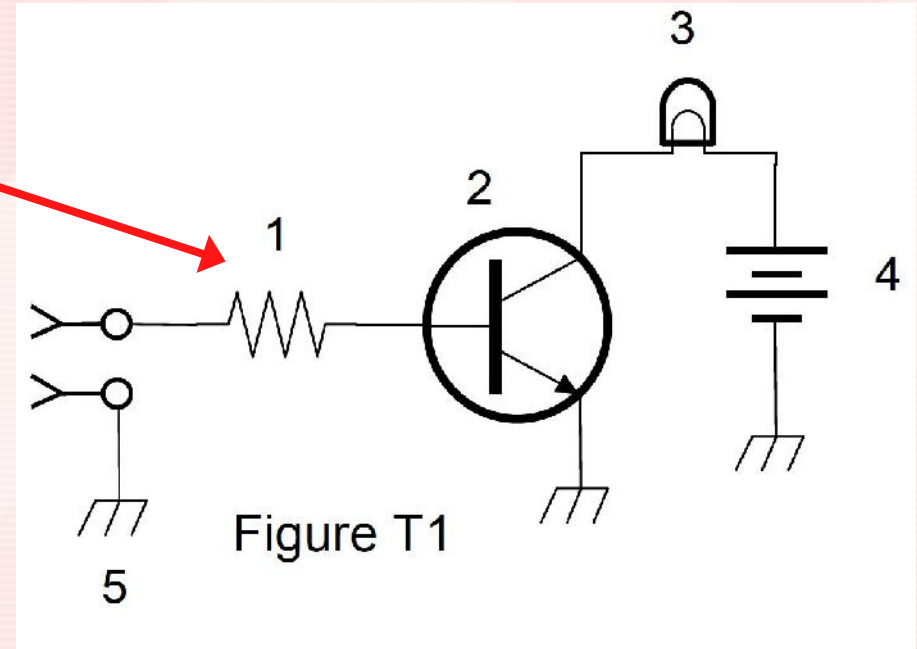- A. Resistor
- B. Transistor
- C. Battery
- D. connector




T6C03 What is component 2 in figure T1?

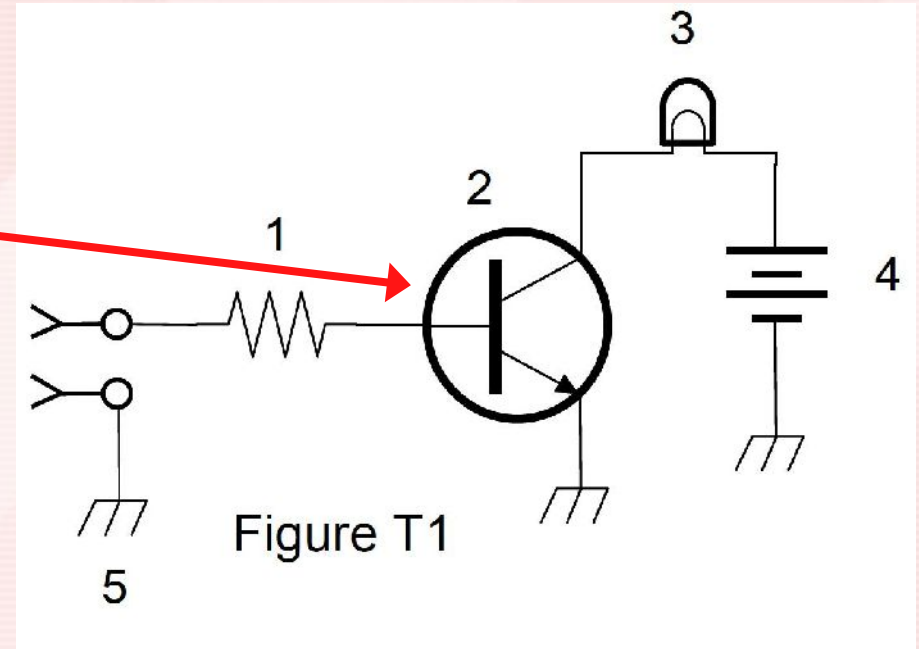- A. Resistor
- B. Transistor
- C. Indicator lamp
- D. Connector




T6D10 What is the function of component 2 in Figure T1?

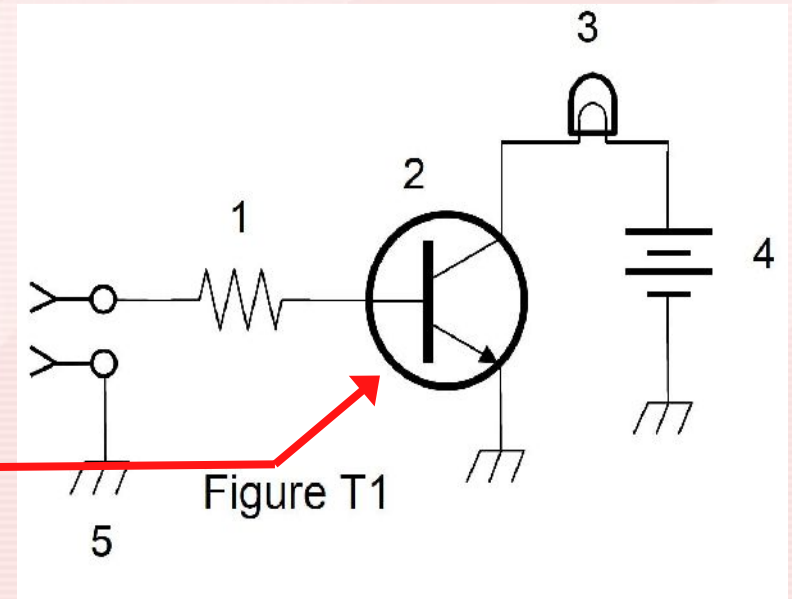- A. Give off light when current flows through it
- B. Supply electrical energy
- C. Control the flow of current
- D. Convert electrical energy into radio waves




T6C04 What is component 3 in figure T1?

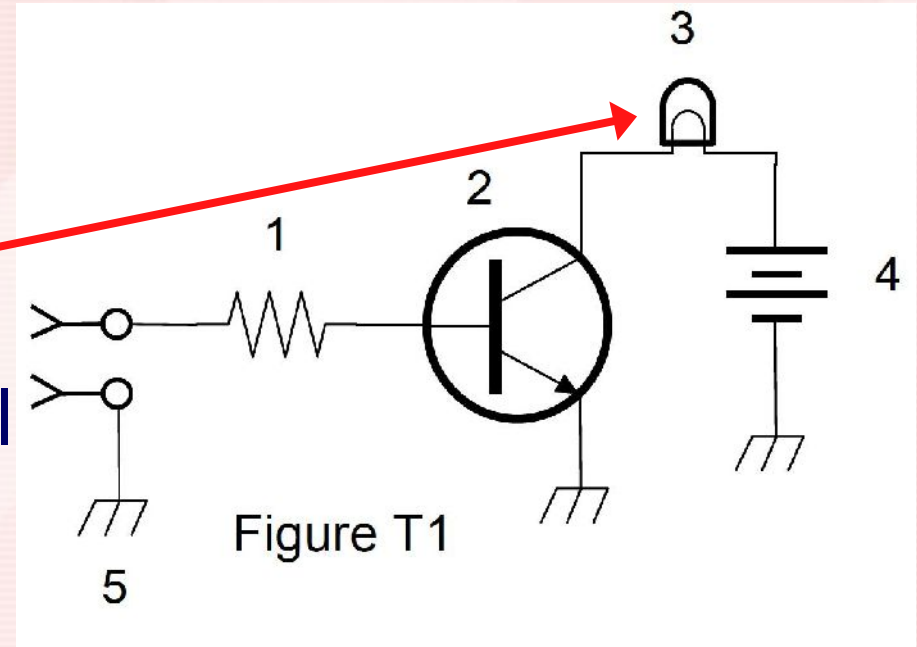- A. Resistor
- B. Transistor
- C. Lamp
- D. Ground symbol



T6C05 What is component 4 in figure T1?

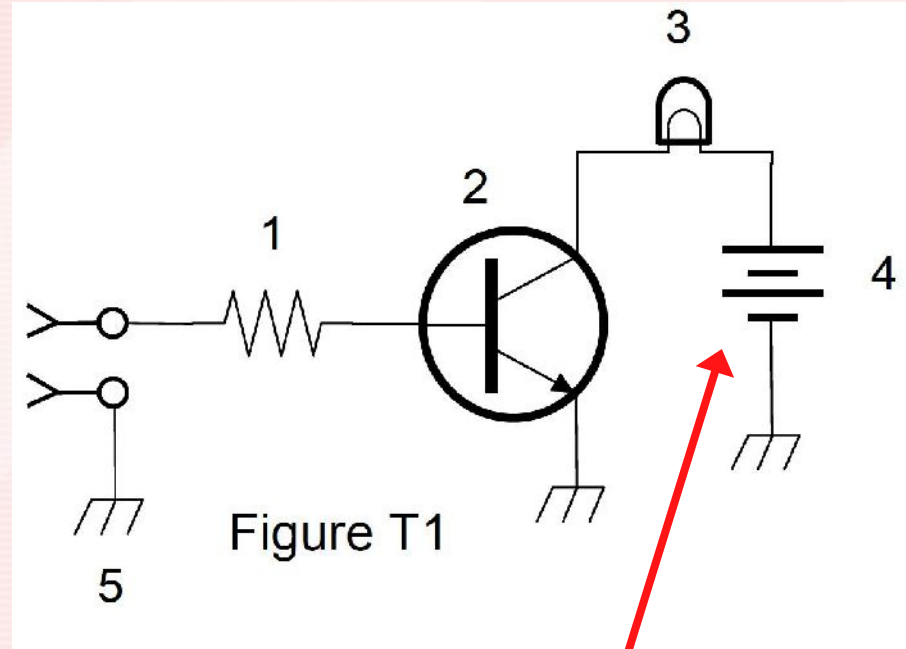- A. Resistor
- B. Transistor
- C. Battery
- D. Ground symbol



T6D03 What type of switch is represented by item 3 in figure T2?

- A. Single-pole single-throw
- B. Single-pole double-throw
- C. Double-pole single-throw
- D. Double-pole double-throw


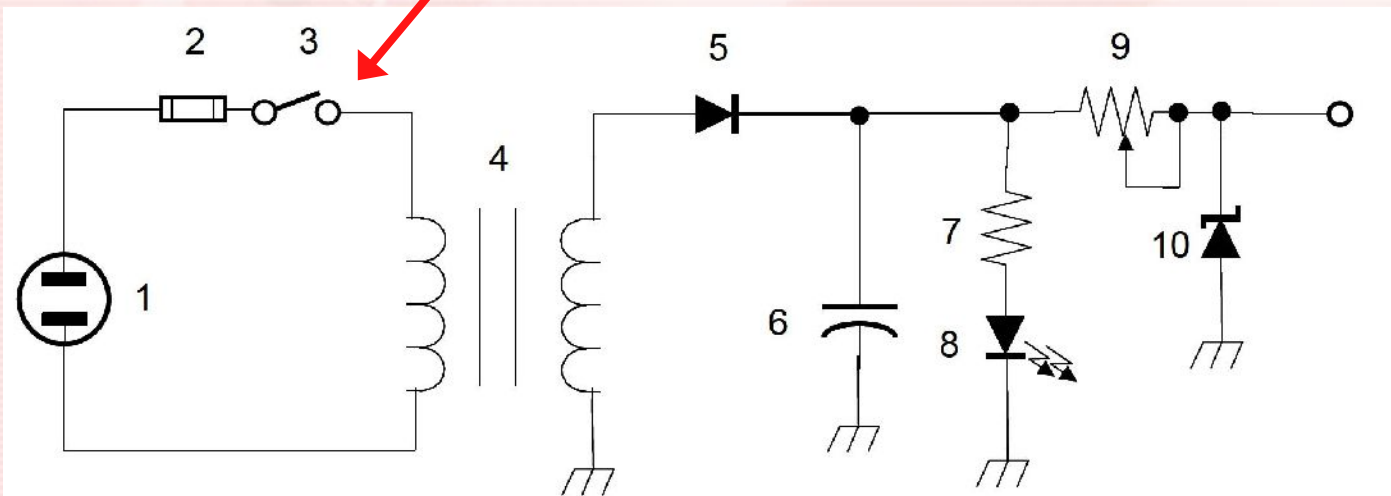


Figure T2

T6C09 What is component 4 in figure T2?

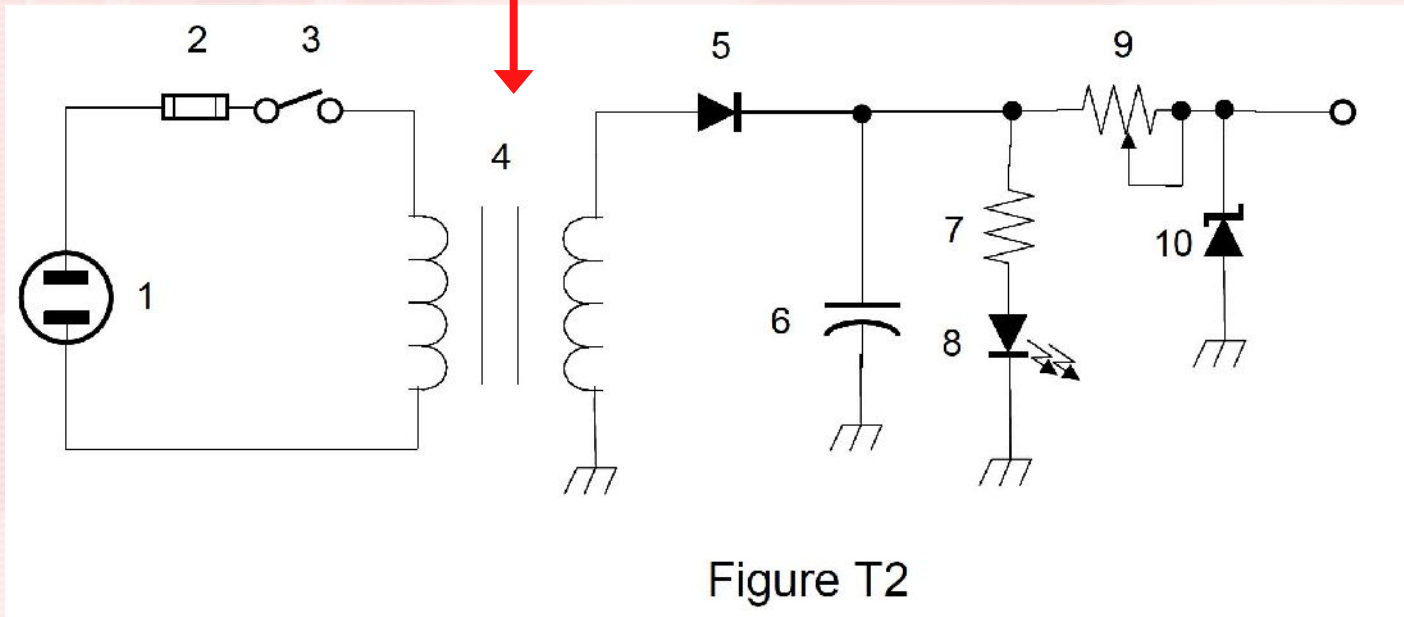- A. Variable inductor
- B. Double-pole switch
- C. Potentiometer
- D. Transformer



T6C06 What is component 6 in figure T2?

- A. Resistor
- B. Capacitor
- C. Regulator IC
- D. Transistor

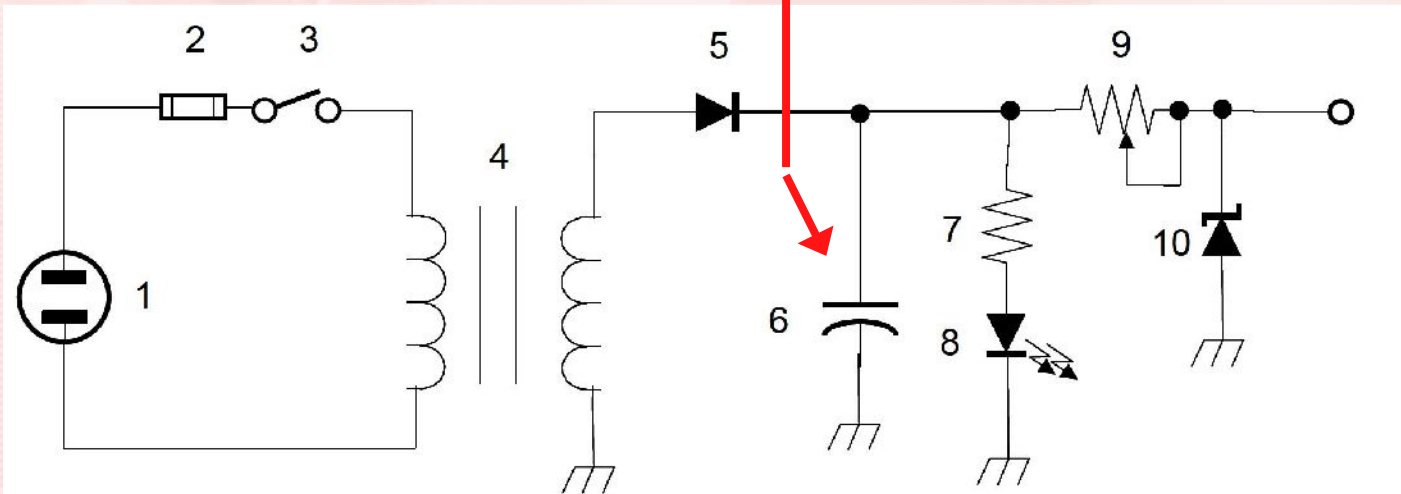


Figure T2

T6C07 What is component 8 in figure T2?

- A. Resistor
- B. Inductor
- C. Regulator IC
- D. Light emitting diode

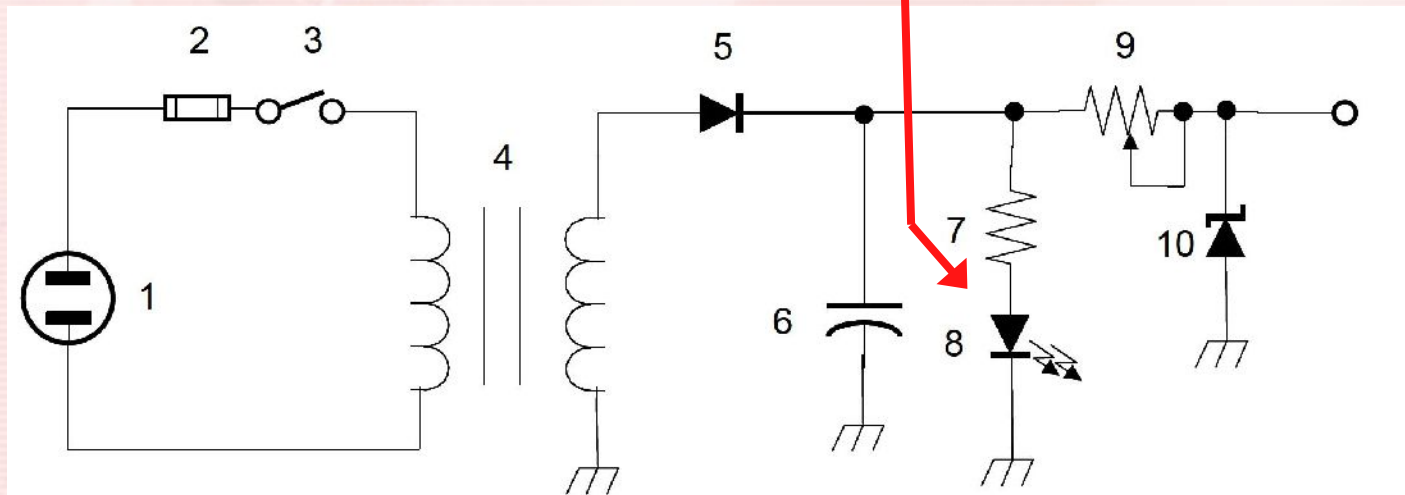


Figure T2

T6C08 What is component 9 in figure T2?

- A. Variable capacitor
- B. Variable inductor
- C. Variable resistor
- D. Variable transformer

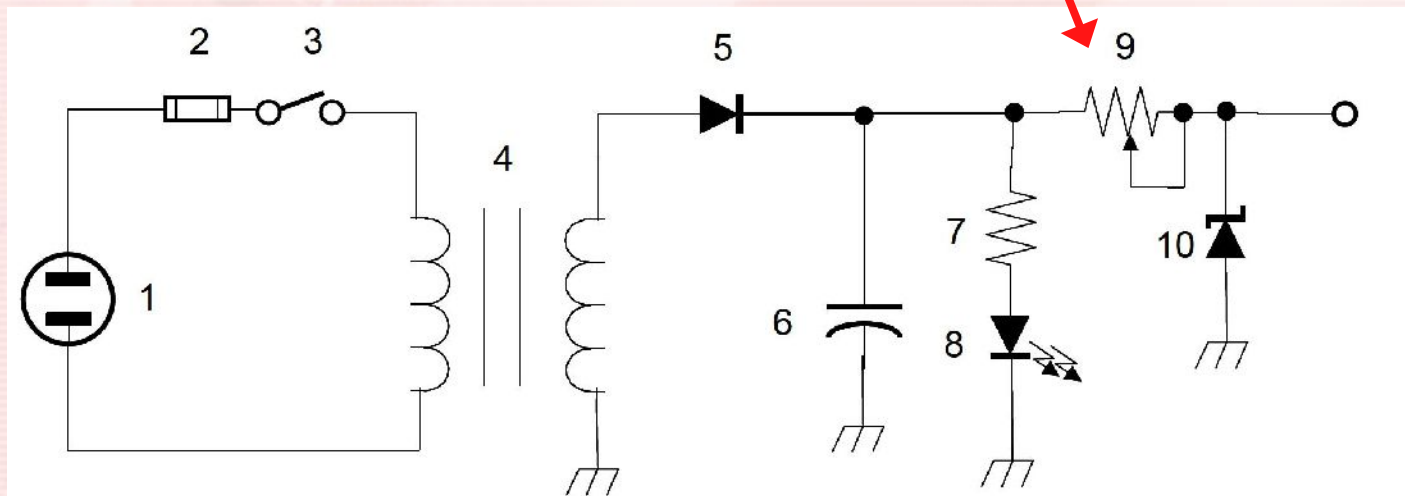


Figure T2

T6D04 Which of the following can be used to display signal strength on a numeric scale?

- A. Potentiometer
- B. Transistor
- C. Meter
- D. Relay

T6D02 What best describes a relay?

- A. A switch controlled by an electromagnet
- B. A current controlled amplifier
- C. An optical sensor
- D. A pass transistor

T5B09

increase

What is the approximate amount of change, measured in decibels (dB), of a power from 5 watts to 10 watts?

- A. 2 dB
- B. 3 dB
- C. 5 dB
- D. 10 dB

T5B10

decrease

What is the approximate amount of change, measured in decibels (dB), of a power from 12 watts to 3 watts?

- A. 1 dB
- B. 3 dB
- C. 6 dB
- D. 9 dB

T5B11

increase

What is the approximate amount of change, measured in decibels (dB), of a power from 20 watts to 200 watts?

- A. 10 dB
- B. 12 dB
- C. 18 dB
- D. 28 dB

T6D05 What type of circuit controls the amount of voltage from a power supply?

- A.** Regulator
- B.** Oscillator
- C.** Filter
- D.** Phase inverter

T6D06

a lower

What component is commonly used to change 120V AC house current to AC voltage for other uses?

- A. Variable capacitor
- B. Transformer
- C. Transistor
- D. Diode

T6D09 What is the name of a device that combines several semiconductors and other components into one package?

- A. Transducer
- B. Multi-pole relay
- C. Integrated circuit
- D. Transformer

T6B07
stand

What does the abbreviation "LED"
for?

- A. Low Emission Diode
- B. Light Emitting Diode
- C. Liquid Emission Detector
- D. Long Echo Delay

T6D07
used

Which of the following is commonly used as a visual indicator?

- A. LED**
- B. FET**
- C. Zener diode**
- D. Bipolar transistor**

15B02 What is another way to specify a radio signal frequency of 1,500,000 hertz?

- A. 1500 kHz
- B. 1500 MHz
- C. 15 GHz
- D. 15 kHz

T5B03 How many volts are equal to one kilovolt?

- A.** One one-thousandth of a volt
- B.** One hundred volts
- C.** One thousand volts
- D.** One million volts

0.003 If an ammeter calibrated in amperes is used to measure a 3000-milliampere current, what reading would it show?

- A. 0.003 amperes
- B. 0.3 amperes
- C. 3 amperes
- D. 3,000,000 amperes

T5B05
500

Which of the following is equivalent to milliwatts?

- A. 0.02 watts
- B. 0.5 watts
- C. 5 watts
- D. 50 watts

T5B01 How many milliamperes is 1.5 amperes?

- A.** 15 milliamperes
- B.** 150 milliamperes
- C.** 1,500 milliamperes
- D.** 15,000 milliamperes

T5B08 How many microfarads are 1,000,000 picofarads?

- A.** 0.001 microfarads
- B.** 1 microfarad
- C.** 1000 microfarads
- D.** 1,000,000,000 microfarads

T5B04 How many volts are equal to one microvolt?

- A.** One one-millionth of a volt
- B.** One million volts
- C.** One thousand kilovolts
- D.** One one-thousandth of a volt

T7D08 Which of the following types of solder is best for radio and electronic use?

- A.** Acid-core solder
- B.** Silver solder
- C.** Rosin-core solder
- D.** Aluminum solder

T7D09 What is the characteristic appearance of a "cold" solder joint?

- A. Dark black spots
- B. A bright or shiny surface
- C. A grainy or dull surface
- D. A greenish tint

T7D07
are

Which of the following measurements commonly made using a multimeter?

- A. SWR and RF power
- B. Signal strength and noise
- C. Impedance and reactance
- D. Voltage and resistance

T7D11 Which of the following precautions should be taken when measuring circuit resistance with an ohmmeter?

- A.** Ensure that the applied voltages are correct
- B.** Ensure that the circuit is not powered
- C.** Ensure that the circuit is grounded
- D.** Ensure that the circuit is operating at the correct frequency

T7D06
damage

Which of the following might
a multimeter?

- A. Measuring a voltage too small for the chosen scale
- B. Leaving the meter in the milliamps position overnight
- C. Attempting to measure voltage when using the resistance setting
- D. Not allowing it to warm up properly

What is probably happening when an ohmmeter, connected across a circuit, initially indicates a low resistance and then shows increasing resistance

with time?

- A. The ohmmeter is defective
- B. The circuit contains a large capacitor
- C. The circuit contains a large inductor
- D. The circuit is a relaxation oscillator